



Digital Logic Design Project



AmirKabir University (AUT-CE)



December 2024


Professor: Dr. Seddighi

Authors: Mohammad Javad Akbari, Parsa Asadi

In the name of God

Introduction

 
This project is designed to implement a car parking system using Verilog. In this project, at the entrance of the parking system, a sensor is used to detect the presence of a vehicle. Once the sensor is triggered and there are some available parking slots, the gate opens to let the vehicle in, otherwise, the gate remains locked. This project is implemented on Spartan 3 board.



Inputs and Outputs


Inputs	Outputs
clk	is_full
entry_sensor	is_open
exit_sensor	capacity [2:0]
exit_slot [1:0]	location [1:0]
reset (active low)	spots [3:0]

System Architecture

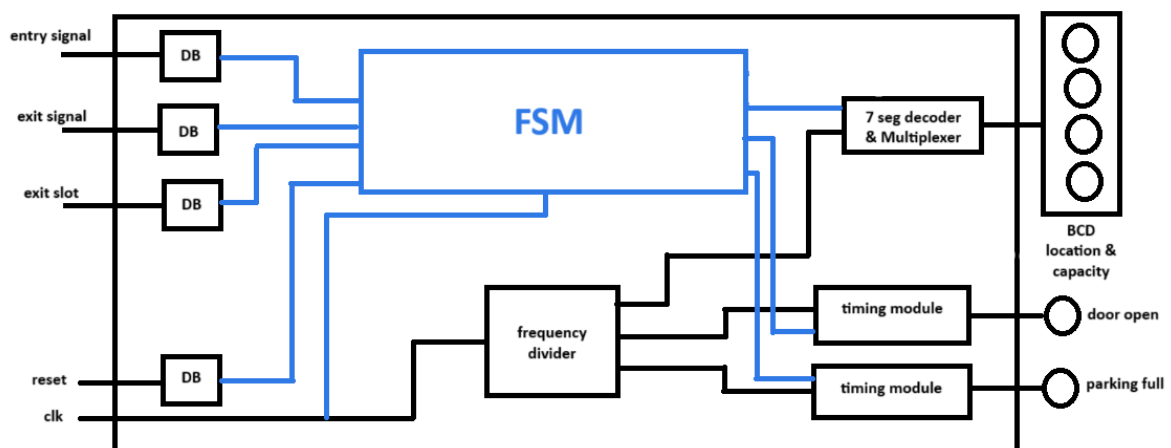

State Diagram (Moore machine)

 This FSM works in 5 main states based on capacity: S0 (Full), S1 (4 cases), S2 (6 cases), S3 (4 cases), S4 (Idle).



Note that this is a simplified diagram. In practice, the machine has 16 cases in total based on parking slots. Output in each state is handled based on memory registers. Some arrows are removed due to simplicity.

FSM in Verilog

```
1. module FSM(
2.   input clk,           // Clock signal
3.   input reset,         // Reset signal (active low)
4.   input entry_signal,  // Signal when a car enters
5.   input exit_signal,   // Signal when a exits
6.   input [1:0] exit_slot, // Selects exiting spot
7.   output reg is_open,  // Signal to open the door
8.   output reg is_full,  // Signal when parking is full
9.   output reg [3:0] spots, // Occupied spots
10.  output reg [2:0] capacity, // Current remaining capacity
11.  output reg [1:0] location // First available empty slot
12. );
13.
14. // Parameters for states based on remaining capacity
15. parameter S4 = 3'b100; // 4 slots remaining (Idle)
16. parameter S3 = 3'b011; // 3 slots remaining
17. parameter S2 = 3'b010; // 2 slots remaining
18. parameter S1 = 3'b001; // 1 slot remaining
19. parameter S0 = 3'b000; // 0 slots remaining (Full)
20.
21. // State change logic
22. always @(posedge clk or reset) begin
23.   if (~reset) begin
24.     capacity = S4;
25.     spots = 4'b0000; // All spots are free (0 = free, 1 = occupied)
26.     is_full = 0;
27.     is_open = 0;
28.     location = 2'b00; // Default to the first slot
29.   end else begin
30.     // State change logic
31.     is_open = 0;
32.     is_full = 0;
33.   end
34.   // Parking management logic
35.   case (capacity)
36.     S4:
37.       if (entry_signal) begin
```

```

38. S3, S2, S1: begin
39. if (entry_signal) begin
40. // Find the first available spot
41. if (spots[0] == 1'b0) location = 2'b00;
42. else if (spots[1] == 1'b0) location = 2'b01;
43. else if (spots[2] == 1'b0) location = 2'b10;
44. else if (spots[3] == 1'b0) location = 2'b11;
45.
46. // fill the spot
47. spots[location] = 1'b1;
48. is_open = 1;
49.
50. end else if (exit_signal) begin
51.
52. // Free the selected spot
53. spots[exit_slot] = 1'b0;
54. is_open = 1;
55.
56. end
57. end
58.
59. S4: begin
60. if (entry_signal) begin
61. // fill the first spot
62. spots[0] = 1'b1;
63. is_open = 1;
64. end
65. end
66.
67. S0: begin
68. if (exit_signal) begin
69. // Free the selected spot
70. spots[exit_slot] = 1'b0;
71. is_open = 1;
72. end
73. end
74.
75. endcase
76.
77. // Next state logic
78. case (capacity)
79. S4: begin
80. if (entry_signal)
81. capacity = S3;
82. end
83.
84. S3: begin
85. if (entry_signal)
86. capacity = S2;
87. else if (exit_signal)
88. capacity = S4;
89. end
90.
91. S2: begin
92. if (entry_signal)
93. capacity = S1;
94. else if (exit_signal)
95. capacity = S3;
96. end
97.
98. S1: begin
99. if (entry_signal)
100. capacity = S0;
101. else if (exit_signal)
102. capacity = S2;
103. end
104.

```

```

105. S0: begin
106. is_full = 1; // Parking is full
107. if (exit_signal)
108. capacity = S1;
109. end
110.
111. endcase
112.
113. end
114. end
115.
116. endmodule
117.

```

FSM testbench in Verilog

```

1. module FSM_TB;
2.
3. // Inputs
4. reg clk;
5. reg reset;
6. reg entry_signal;
7. reg exit_signal;
8. reg [1:0] exit_slot;
9.
10. // Outputs
11. wire is_open;
12. wire is_full;
13. wire [3:0] spots;
14. wire [2:0] capacity;
15. wire [1:0] location;
16.
17. // Instantiate the ParkingSystem module
18. FSM uut (
19. .clk(clk),
20. .reset(reset),
21. .entry_signal(entry_signal),
22. .exit_signal(exit_signal),
23. .exit_slot(exit_slot),
24. .is_open(is_open),
25. .is_full(is_full),
26. .spots(spots),
27. .capacity(capacity),
28. .location(location)
29. );
30.
31. // Clock generation
32. always #5 clk = ~clk;
33.
34. // Test sequence
35. initial begin
36. // Initialize inputs
37. clk = 0;
38. reset = 0;
39. entry_signal = 0;
40. exit_signal = 0;
41. exit_slot = 2'b00;
42.
43. // Enable machine
44. #10 reset = 1;
45.
46. // Test case 1: First car enters
47. #10 entry_signal = 1;
48. #10 entry_signal = 0; // Simulate a short entry pulse

```

```

49.
50. // Test case 2: Second car enters
51. #10 entry_signal = 1;
52. #10 entry_signal = 0;
53.
54. // Test case 3: Third car enters
55. #10 entry_signal = 1;
56. #10 entry_signal = 0;
57.
58. // Test case 4: Fourth car enters (parking is full)
59. #10 entry_signal = 1;
60. #10 entry_signal = 0;
61.
62. // Check is_full signal
63. #10;
64.
65. // Test case 5: A car exits from slot 2
66. #10 exit_signal = 1;
67. exit_slot = 2'b10; // Specify the slot
68. #10 exit_signal = 0;
69.
70. // Test case 6: Another car enters
71. #10 entry_signal = 1;
72. #10 entry_signal = 0;
73.
74. #50;
75. $finish;
76. end
77.
78. endmodule
79.

```

FSM testbench simulation result

